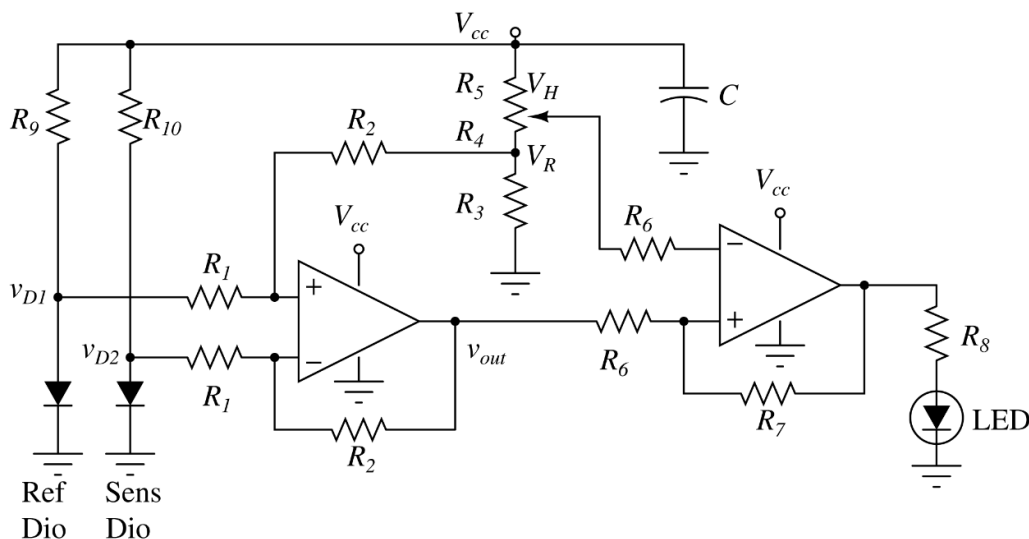


EE313 Laboratory #1 (v2)

Diode Characterization and Differential Temperature Sensor

- A. Design a method to measure I_s of a p-n diode, 1N4148. The diode current is given by $I_D = I_s(e^{V_D/(nV_T)} - 1)$ where $n=1.752$ and $V_T=kT/q$. For 1N4148, the maximum current should never exceed 50mA.
- B. Design a differential temperature sensor using the temperature dependence of a diode forward voltage under constant current with the following specifications (all components in the room temperature, between 18°C to 28°C.). You may use the circuit recommended below (diodes are 1N4148. OPAMPs are LM358, two OPAMPs in the same package). You should use a single supply voltage of $V_{cc} = \text{mod}(\text{BilkentID}, 5) + 10\text{V}$. [$\text{mod}(xx, 5)$ is the remainder of xx after division by 5.]



Choose R_9 and R_{10} so the reference and sensor diodes have a current of about $I_D = 1\text{mA}$.

$$R_9 = R_{10} = (V_{cc} - 0.6) / (I_D).$$

The analysis of the difference amplifier gives:

$$v_{out} = (R_2/R_1)(v_{D1} - v_{D2}) + V_R$$

The comparator analysis gives the two threshold voltages:

To turn on the LED, $v_{out} > V_H(R_7 + R_6)/R_7$.

To turn off the LED, $v_{out} < V_H(R_7 + R_6)/R_7 - (R_6/R_7)(V_{cc} - 2)$

Hence, the hysteresis value is $(R_6/R_7)(V_{cc} - 2)$.

Choose $V_R = V_{cc} R_3 / (R_3 + R_4 + R_5)$ assuming $R_2 \gg R_3$ (e.g., $R_2 \geq 20 R_3$)

Use a multiturn pot of 10K for $R_4 + R_5$ for a fine adjustment of V_H :

$$V_H = V_{cc} (R_3 + R_4) / (R_3 + R_4 + R_5)$$

Choose (R_2/R_1) to give the required gain.

Choose the LED current limiting resistor to generate an LED current of 10mA: $R_8 \approx (V_{cc} - 4) / 0.01$

Choose the values of resistors so that they are all standard values (1, 1.2, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2). If you need to tune a value, insert a parallel resistor (rather than a series resistor).

1. When both diodes are at room temperature ($v_{D1}=v_{D2}$), the output voltage, v_{out} , should be at $(V_{cc}-2)/4$
2. The output voltage should show the temperature difference between the room temperature and the temperature of the sensor diode in degrees with a 10% tolerance. For example, if the sensor diode is +1-degree warmer, v_{out} should change by +1V.
3. A red LED should turn on when the sensor's temperature exceeds $+5\pm0.5^\circ\text{C}$ the room temperature.
4. The LED should never flicker around the thresholds: It should have a 0.1°C (0.1V) hysteresis.

Preliminary work (Due Sept. 29, 2024)

- A. Simulate your method using LTSpice to determine the I_s of the diode.
- B. Show using LTSpice and 1N4148 diode, that I_s value found is nearly equal to the spice model value of 2.52nA. Note that 1N4148 diode is modeled in LTSpice as $I_d=I_s (e^{V_d/(nV_T)}-1)$ where $n=1.752$ and $V_T=kT/q$.
- C. Using LTSpice, show that when both sensors are at 18°C and 28°C , the output voltage is nearly $(V_{cc}-2)/4 \pm 0.3\text{V}$.
- D. Using LTSpice, show that the output voltage, v_{out} , increases by $1\pm0.1 \text{ V}/^\circ\text{C}$ by sensor temperature when the room temperature is at 23°C .
- E. Using LTSpice, show that LED voltage goes high when the sensor's temperature increases to $+5\pm0.5^\circ\text{C}$ above the room temperature of 23°C . You can use the L128-DRD1003500000 component in LTSpice diode library with a current limiting resistor, R_s , in series. LED is assumed to be on when a current flows through it.
- F. Using LTSpice, show that LED voltage goes low when the sensor's temperature is reduced to 0.1°C below its turn-on point.

The default temperature of simulation in LTSpice is 27°C . This can be changed, for example, to 22°C by adding the spice directive

.temp 22

LTSPICE allows the device temperature of a component to be set. However, this possibility is not described in the documentation. Control right-click on the diode body and add "temp={t1}" to one of the empty attribute fields after the diode model name (for example, Value2). Then add

.step param t1 begin end stepsize

Spice directive to see the response as a set of curves with different temperatures.

Provide a schematic of your design, showing a component list. Use Diptrace to generate the schematic. Refer to the Diptrace Tutorial.

Upload your report containing the schematic as a pdf file. Then upload the LTSpice .asc file.

Experimental work (Due Oct. 6, 2024)

- A. Apply your method to measure I_s of a 1N4148 diode.

- B. Build your temperature sensor design on a breadboard. You may use a resistor in physical contact with the sensor diode and insulate it with electrical tape to adjust the sensor temperature. The resistor may be connected to a separate adjustable voltage source to heat the sensor in a controlled manner. Connect your multimeter to the output. Show that it satisfies all the specifications. It is always a good idea to place a decoupling capacitor ($C=100\text{nF}$) between the supply voltage and the ground. You may use a thermocouple provided with many multimeters to measure the room and sensor temperatures and calibrate the resistive heater.

Upload pdf report.

Grading criteria:

Preliminary work (10 pts)

I_s measurement method with LTSpice simulation: 1pt

Nice looking temperature sensor schematic with component list: 1pt

Satisfaction of all four criteria in LTSpice: 8pts, 2 pts each

Experimental work (10 pts)

I_s measurement: 1pt

A neat, easy-to-follow, and easy-to-debug circuit implementation on the breadboard. 1pt

Experimental satisfaction of all four criteria: 8 pts, 2pts each