

EEE 313 - Electronic Circuit Design - Lab 3 Preliminary Report

Tuna Şahin - Single-Supply Push-pull Class-B Power Amplifier

Introduction:

For this lab, we were asked to design a Single-Supply Push-Pull Class-B Power Amplifier. In order to do so, we used a complementary BJT approach. My Bilkent ID is 22201730, so I was asked to implement the amplifier with a gain of $20 + \text{mod}(22201730, 7) = 25\text{dB}$.

Calculations:

1. We needed to choose $C_5 \ll R_L$ at 150Hz. To do so we evaluated the following

inequality. $\frac{1}{j\omega C} < 33\Omega$, Choosing $C_5 = 270\mu F$ allowed us to get $X_C \simeq 24\Omega$ at 150Hz.

2. We needed to choose R_2 and R_3 so that $I_C(Q4) = 10I_{R3}$

$$I_{R3} = \frac{R_3 I_{R3} - 24}{R_2} - I_B \text{ and } I_B = V_{CC} - V_{BE} - 27(\beta + 1)I_B - I_{R3}R_3 \text{ and } \beta I_B = 10I_{R3}$$

Arbitrarily choosing $R_2 = 1k$ and solving these equations gives us $R_3 \simeq 22k$

3. Assuming $V_{BE} = 0.7$ we need to choose R_{10} and R_{11} such that:

$$1 \leq (1 + \frac{R_{10}}{R_{11}})0.7 \leq 1.1 \Rightarrow 0.428 \leq \frac{R_{10}}{R_{11}} \leq 0.571$$

I chose $R_{10} = 2.7k$ and $R_{11} = 5.6k$ so $R_{10}/R_{11} = 0.5$

4. R_4 and R_5 control the gain of the Opamp. They are chosen as $R_5 = 1.5k$ and $R_4 = 27k \parallel 450k$

LTSpice Simulations:

Our designs had some criteria they needed to satisfy.

1. The amplifier should deliver at least 0.95W power to a 33Ω resistance (16Vpp to a 33Ω power resistor) at 1KHz with the chosen gain value.


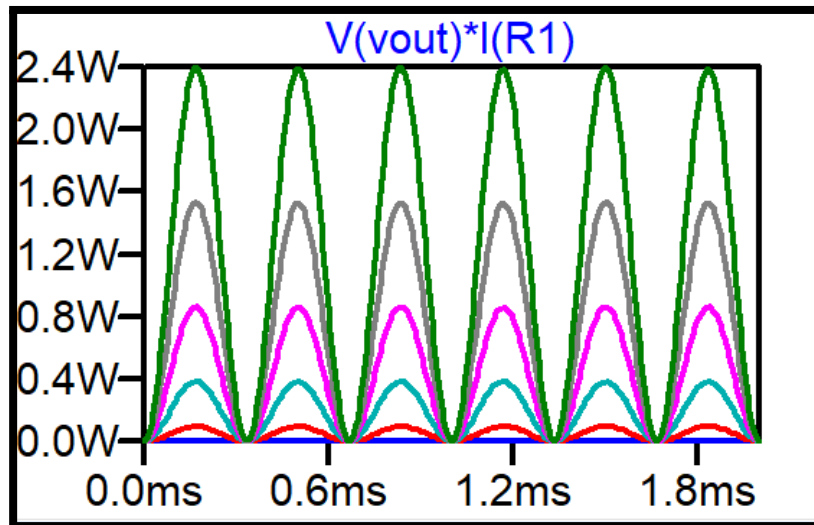


Figure 1.1: Load Power Consumption

The circuit can deliver up to 2.4W to the load at 1kHz.

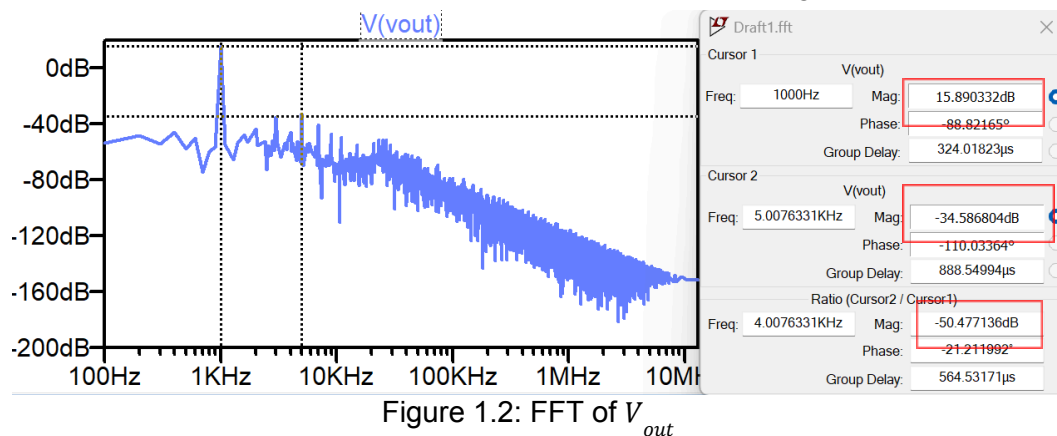2. The harmonics (the highest is possibly the third harmonic) at the 0.95W output power level should be at least 40 dB lower than the fundamental signal at 1 KHz.



The third harmonic, which was indeed the highest, is 50dB lower than the fundamental harmonic.

3. The power consumption at quiescent conditions should be less than 500mW.

Measurement: pin	
step	AVG(-v(vcc)*i(v1))
1	0.365081
2	0.762372
3	1.17112
4	1.57973
5	1.98815
6	2.39598

Figure 1.3: P_{in} when $V_{in} = 0$

The quiescent power consumption is 360mW. (when $V_{in} = 0$)

4. The amplifier's efficiency (output power/total supply power) should be at least 40% at max power output (0.95W) at 1KHz.

Measurement: efficiency	
step	pout/pin
1	1.45612e-21
2	0.0628287
3	0.163489
4	0.272649
5	0.385114
6	0.49953

Figure 1.4: Efficiency at max power

5. The -3dB bandwidth of the amplifier should be at least 150Hz to 15KHz.a

Measurement: gain		Measurement: gain		Measurement: gain	
step	20*log10(v)	step	20*log10(v)	step	20*log10(v)
1	inf	1	inf	1	inf
2	24.9266	2	25.0065	2	24.8449
3	24.9252	3	25.0047	3	24.8337
4	24.9264	4	24.9922	4	24.806
5	24.9265	5	24.988	5	24.6781
6	24.9278	6	24.988	6	24.0967

Figure 1.5: Gain values at $f = 150\text{Hz}$, $f = 1\text{kHz}$, $f = 15\text{kHz}$

The gain at 150Hz, 1kHz, 15kHz is 24.92dB, 25dB, and 24dB respectively.

LTSpice Schematic:

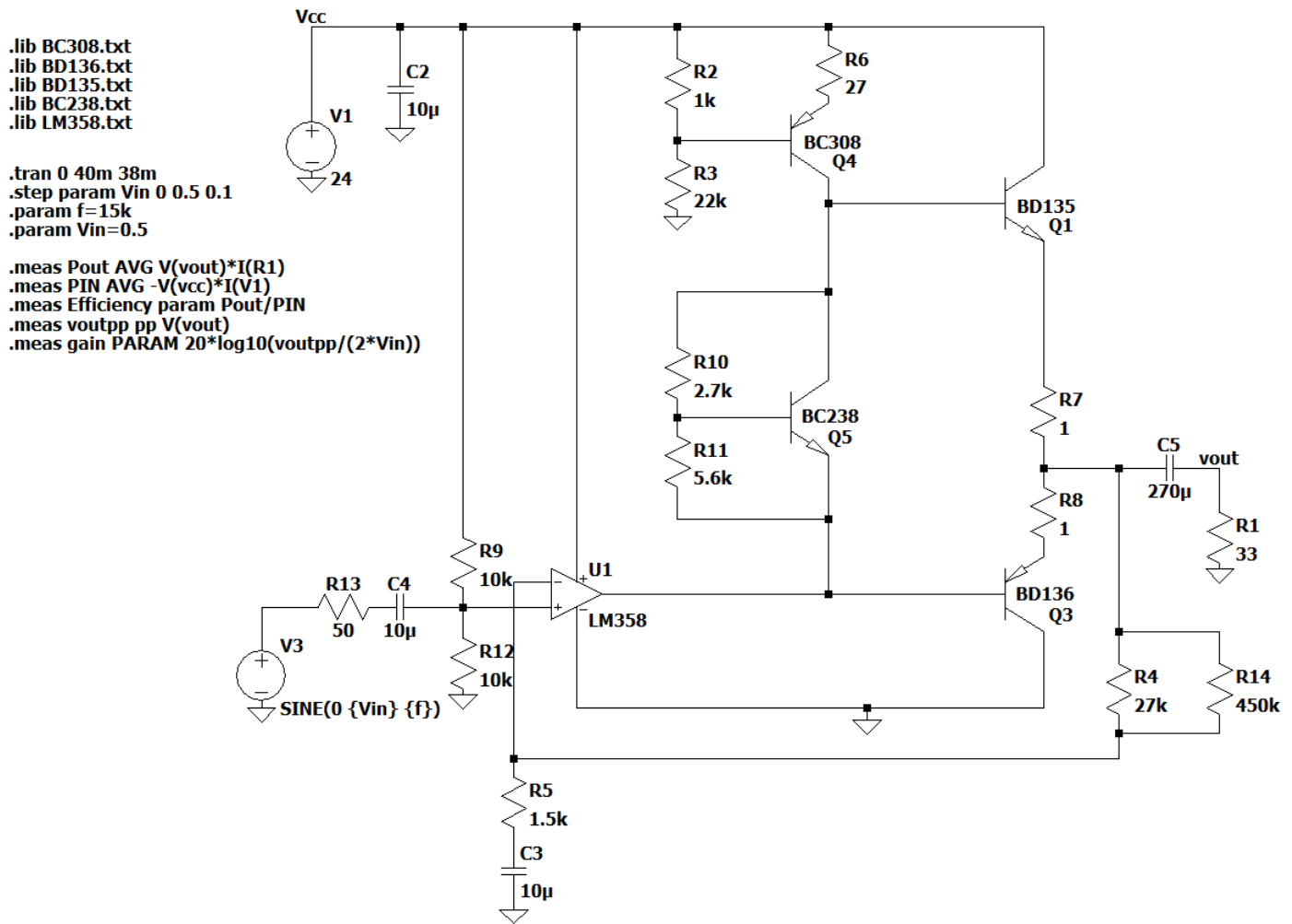


Figure 2: LTSpice Schematic

Diptrace Schematic:

